

Example #5: Determine the unknown voltages for each of the following circuits.

